

ECE M216A Project, Fall 2024  
December 7, 2024

Group #8 Team Members:  
Maxwell Jung, maxwelljung@ucla.edu  
Peter Pincencia, pmp1208@g.ucla.edu  
~~Chris Valencia, Chrsv@gmail.com~~ (dropped course)

**Performance Summary**

Max Fclk (MHz)	Area ( $\mu\text{m}^2$ )	Energy (pJ)	Hold Time Slack (ps)	EA/f	Tclk (1/Fclk)
2173.91	4213.15	1.25	0.01303	2.42	0.46ns


Math can be checked here: <https://www.desmos.com/calculator/neb4eqn1uy>

Github: <https://github.com/MaxwellJung/ecem216a>

See next page for architecture.

## Architecture

### Block Diagram

 

### Key Features

Increase throughput (2+GHz) by inserting registers to break long combinational logic

### Modules

- latency
  - Chain of registers to delay signal by N clock cycles
- program\_height\_to\_id
  - Computes up to 3 possible strips a program can fit into
    - First strip ID (`strip_id_0`) corresponds to higher priority then second strip ID (`strip_id_1`) which is higher priority then third strip ID (`strip_id_2`)
    - Strip ID indexed from 1 to 13
      - ID of 0 corresponds to null/error
  - Combinational logic
- least\_strip
  - Priority comparator
    - Compares 3 strip IDs and their corresponding widths and outputs the best strip ID and width

- If widths are equal, break ties in the order  $\text{strip\_id\_0} < \text{strip\_id\_1} < \text{strip\_id\_2}$
  - Clocked with latency of 2 clock cycles to increase throughput
- `id_to_y`
  - Converts strip id to y position on compute array
  - Combinational
- Counter (not shown above)
  - Counts from 1 to 4 to track number of clock cycles since program arrival
  - Output value used to synchronize different register writes

### **Synchronization**

All register writes are synchronized using the value from the counter.

Inputs are registered (consuming 1 clock cycle), then delayed by 2 more clock cycles using the latency module.

On the 4th clock cycle, the height of the program is converted into 3 potential strip IDs.

On the 5th and 6th clock cycle, the best strip out of the 3 potential strips is chosen (valid output on 6th clock cycle).

On the 7th clock cycle, the y position of the strip and the new width of the chosen strip is computed.

On the 8th clock cycle, the new width is written to memory (`strip_widths`) and the outputs are registered.